 



General Model of Synchronous Circuit



- All wires, except clock, may be multiple bits wide.
 - Combinational Logic Blocks (CL)
 - no internal state
 - output only a function of inputs
- Registers (reg)
 - collections of flip-flops
- clock
 - distributed to all flip-flops
 - typical rate?
- Particular inputs/outputs are optional
 - Optional Feedback


Example Circuit

- Parallel to Serial Converter

 

- All signal paths single bit wide
- Registers are single flip-flops
- Combinational Logic blocks are simple multiplexors
- No feedback in this case.


General Model of Synchronous Circuit

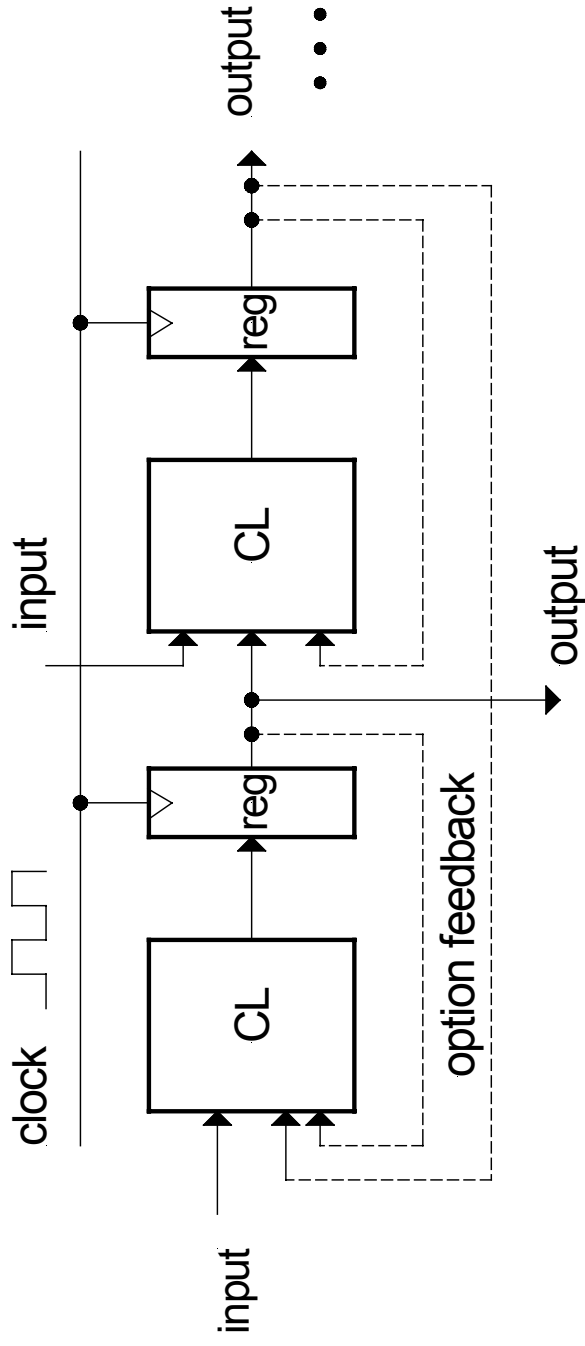

- How do we measure performance?
 - operations/sec?
 - cycles/sec?
- What limits the clock rate?
- What happens as we increase the clock rate?


Limitations on Clock Rate

1 Logic Gate Delay

 

- What are typical delay values?



2 Delays in flip-flops

 


- Both times contribute to limiting the clock period.
- What must happen in one clock cycle for correct operation?
- Assuming perfect clock distribution (all flip-flops see the clock at the same time):
 - All signals must be ready and “setup” before rising edge of clock.

Example

- Parallel to serial converter:

  

General Model of Synchronous Circuit

 

- In general, for correct operation:

$$T \geq \text{time}(\text{clk} \rightarrow Q) + \text{time}(\text{CL}) + \text{time}(\text{setup})$$

$$T \geq \tau_{\text{clk} \rightarrow Q} + \tau_{\text{CL}} + \tau_{\text{setup}}$$


for all paths.

- How do we enumerate *all paths*?


- Any circuit input or register output to any register input or circuit output.
- “setup time” for circuit outputs depends on what it connects to
- “clk-Q time” for circuit inputs depends on from where it comes.

Clock Skew


- Unequal delay in distribution of the clock signal to various parts of a circuit:
 - if not accounted for, can lead to erroneous behavior.
 - Comes about because:
 - clock wires have delay,
 - circuit is designed with a different number of clock buffers from the clock source to the various clock loads, or
 - buffers have unequal delay.
 - All synchronous circuits experience some clock skew:
 - more of an issue for high-performance pipelined designs operating with very little extra time per clock cycle.

 


Clock Skew (cont.)

 

- If clock period $T = T_{CL} + T_{\text{setup}} + T_{\text{clk} \rightarrow Q}$, circuit will fail.
- Therefore:
 1. Control clock skew
 - a) Careful clock distribution. Equalize path delay from clock source to all clock loads by controlling wires delay and buffer delay.
 - b) don't "gate" clocks.
 2. $T \geq T_{CL} + T_{\text{setup}} + T_{\text{clk} \rightarrow Q}$ + worst case skew.
- Most modern large high-performance chips (microprocessors) control end to end clock skew to a few tenths of a nanosecond.

 

Clock Skew (cont.)

 

- Note reversed buffer.
- In this case, clock skew actually provides *extra time* (adds to the effective clock period).
- This effect has been used to help run circuits as higher clock rates. Risky business!